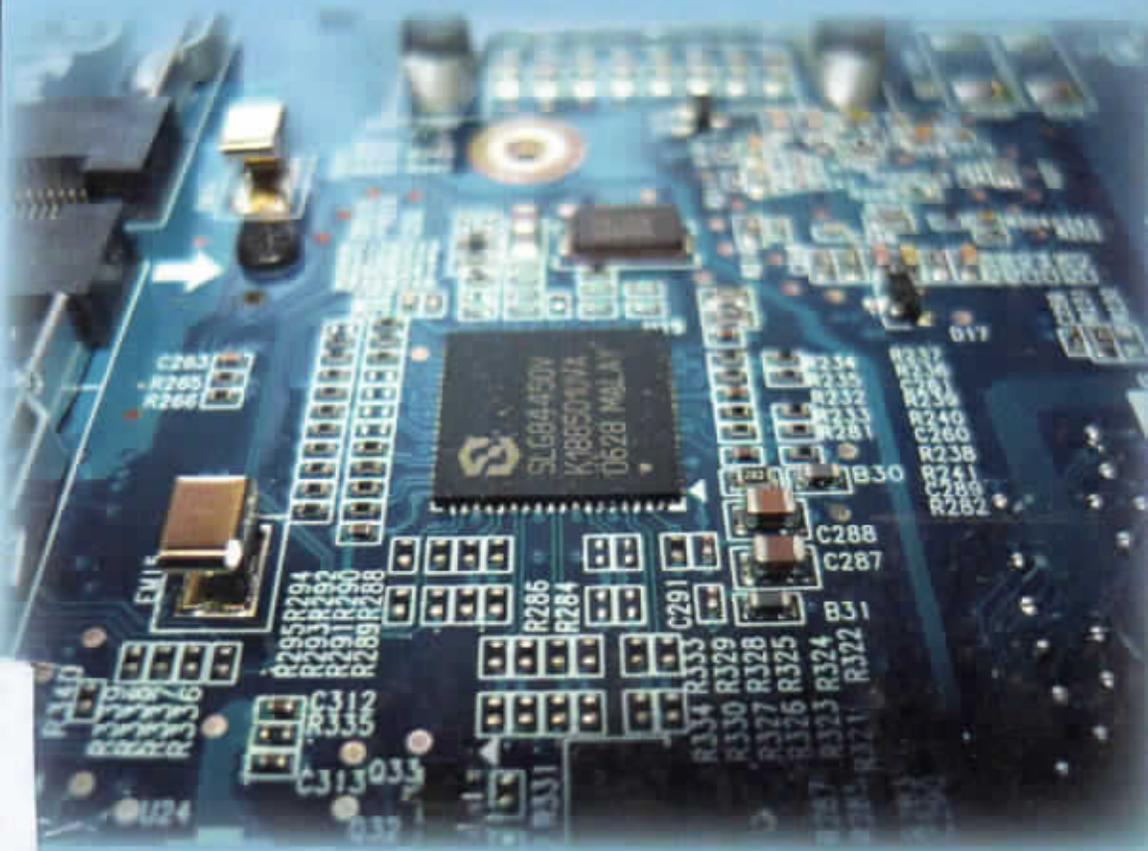


CIRCUIT THEORY



Rf
621.3772
C778
2014
f

62-1790

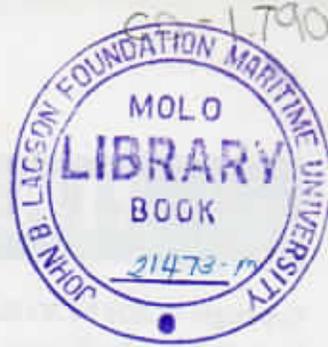


TABLE OF CONTENTS

CIRCUIT THEORY

Chapter 1: Introduction	1
Chapter 2: DC Circuit Analysis	15
Chapter 3: AC Circuit Analysis	45
Chapter 4: Power in AC Circuits	75
Chapter 5: Frequency Response	105
Chapter 6: Two-Port Networks	135
Chapter 7: Laplace Transform	165
Chapter 8: Z-Transform	195
Chapter 9: State-Space Analysis	225
Chapter 10: Filter Design	255
Chapter 11: Operational Amplifiers	285
Chapter 12: Feedback Amplifiers	315
Chapter 13: Oscillators	345
Chapter 14: Digital Circuits	375
Chapter 15: Microprocessors	405
Chapter 16: Communication Systems	435
Chapter 17: Antennas	465
Chapter 18: Wave Propagation	495
Chapter 19: Fiber Optics	525
Chapter 20: Microwave Engineering	555
Chapter 21: Satellite Communication	585
Chapter 22: Mobile Communication	615
Chapter 23: Wireless LANs	645
Chapter 24: Broadband Wireless	675
Chapter 25: Introduction to RF	705
Chapter 26: Antenna Fundamentals	735
Chapter 27: Antenna Arrays	765
Chapter 28: Antenna Measurements	795
Chapter 29: Antenna Design	825
Chapter 30: Antenna Applications	855
Chapter 31: Antenna Theory	885
Chapter 32: Antenna Synthesis	915
Chapter 33: Antenna Modeling	945
Chapter 34: Antenna Simulation	975
Chapter 35: Antenna Optimization	1005
Chapter 36: Antenna Design Tools	1035
Chapter 37: Antenna Design Examples	1065
Chapter 38: Antenna Design Projects	1095
Chapter 39: Antenna Design References	1125
Chapter 40: Antenna Design Bibliography	1155



3G eLEARNING

TABLE OF CONTENTS

1. Basic Circuits Analysis	
1.1 Basics Of Circuits.....	1
1.1.1 Active and Passive Element	1
1.2 Kirchoff's Law	9
1.3 Mesh and Nodal Analysis	9
2. Network Reduction And Network Theorems	
2.1 Theorems	23
2.1.1 Superposition	23
2.1.2 Thevenin's Theorem.....	30
2.1.3 Norton's Theorem.....	31
2.1.4 Maximum Power Transfer Theorem.....	35
2.1.5 Reciprocity Theorem.....	35
2.1.6 Tellegen's Theorem.....	36
2.1.7 Millman's Theorem.....	36
2.1.8 Star-To-Delta Conversion	38
2.1.9 Delta-to-star Conversion.....	39
2.2 One Port and Two Port Network Functions	40
2.2.1 Properties of driving point impedance and admittance functions	43
2.2.2 Network Transform Functions	43
2.2.3 Impedance Matrix of Gyrator.....	44
2.2.4 Z or Impedance parameters.....	45
2.2.5 Y or Admittance Parameter.....	47
2.2.6 Hybrid (h) Parameters.....	48
2.2.7 Inverse Hybrid Parameter (g-parameter).....	48
2.2.8 Transmission Parameters (ABCD-parameters)	48
2.2.9 Cascading.....	49
3. Circuit Switching	
3.1 Simple Switching Network	54
3.1.1 Circuit Switching Networks	56
3.2 Circuit Switching Concepts	56
3.2.1 Space Division Switching	57
3.2.2 Time Division Multiplexing.....	60
3.3 Control Signalling	62
3.3.1 Channel and Common Channel Signalling	63
3.4 Brief Idea of SS7.....	65
3.4.1 Advantages of SS7	66
3.5 Packet Switching.....	67
3.5.1 Packet- Switching Principles	70
3.6 Routing in Switching Networks	71
3.6.1 Routing in Circuit Switching Network.....	71
3.6.2 Routing in Packet Switching Networks	72
3.7 X.25 in Computer Networking.....	73
3.7.1 X.25 Applications	74
4. Transient Response	
4.1 Transistor Construction	77
4.2 Transistor Operation	78
4.3 Common-Base Configuration.....	81
4.3.1 Alpha (α).....	87
4.3.2 Biasing	88
4.4 Transistor Amplifying Action	88
4.5 Common-Emitter Configuration	90
4.5.1 Beta (β).....	94

4.5.2	Biasing	99	5.7.1	Design of a Bias Circuit with an Emitter Feedback Resistor	172
4.6	Common-Collector Configuration	101	5.7.2	Design of a Current-Gain- Stabilized (Beta-Independent) Circuit	173
4.7	Limits of Operation	102	5.8	Transistor Switching Networks	175
4.8	Transistor Specification Sheet	105	5.9	Troubleshooting Techniques	182
4.9	Transistor Testing	110	5.10	pnp Transistors	187
4.9.1	Curve Tracer	110	5.11	Bias Stabilization	191
4.9.2	Transistor Testers	111	5.11.1	Stability Factors $S(ICO)$, $S(VBE)$, and $S(\beta)$	192
4.9.3	Ohmmeter	112	5.11.2	$S(ICO)$: Emitter-Bias Configuration	194
4.10	Transistor Casing and Terminal Identification	114	5.11.3	Fixed-Bias Configuration	196
5.	Transistor Characteristics		5.11.4	Voltage-Divider Bias Configuration	197
5.1	Operating Point	117	5.11.5	Feedback-Bias Configuration (RE 5.0 V)	197
5.2	Fixed-Bias Circuit	120	5.11.6	Physical Impact	198
5.2.1	Forward Bias of Base-Emitter	122	5.11.7	$S(VBE)$	200
5.2.2	Collector-Emitter Loop	122	5.11.8	$S(\beta)$	203
5.2.3	Transistor Saturation	126	5.11.9	Summary	204
5.2.4	Load-Line Analysis	128	5.12	Practical Applications	206
5.3	Emitter Bias	132	5.12.1	Relay Driver	206
5.3.1	Base-Emitter Loop	133	5.12.2	Transistor Switch	207
5.3.2	Collector-Emitter Loop	136	5.12.3	Constant-Current Source (CCS)	208
5.3.3	Improved Bias Stability	138	5.12.4	Alarm System with a CCS	210
5.3.4	Saturation Level	139	5.12.5	Logic Gates	212
5.3.5	Load-Line Analysis	140	5.12.6	Current Mirror	214
5.4	Voltage-Divider Bias	141	5.12.7	Voltage Level Indicator	216
5.4.1	Exact Analysis	143	6.	Three Phase Circuits	
5.4.2	Approximate Analysis	146	6.1	Neutral Currents in Three Phase Wye Systems	221
5.4.3	Transistor Saturation	151	6.1.1	Wye and Delta Configurations	223
5.4.4	Load-Line Analysis	152	6.1.2	Voltage, Current, and Power Measurements in a Wye-Connected Circuit	223
5.5	DC Bias with Voltage Feedback	152			
5.5.1	Base-Emitter Loop	152			
5.5.2	Collector-Emitter Loop	155			
5.5.3	Saturation Conditions	158			
5.5.4	Load-Line Analysis	158			
5.6	Miscellaneous Bias Configurations	159			
5.7	Design Operations	167			

6.1.3	Voltage, Current, and Power Measurements in a Delta-Connected Circuit	224	6.4	Delta Connection	233
6.2	Measurement of Three-phase Power	227	6.4.1	Wye and Delta Comparison	234
6.2.1	The Two-Wattmeter Method	228	6.4.2	Power Measurements	235
6.2.2	Neutral Current in an Unbalanced Three-phase Load	229	6.4.3	Configuring Measurement Equipment	237
6.2.3	Advantages of Three-phase Systems	229	6.5	Power System Fault Analysis	238
6.3	The Fundamentals of Three-Phase Power Measurements	230	6.5.1	Derivation of Sequence Networks	240
6.3.1	Three-Phase Systems	230	6.6	Voltage Unbalance on the Performance of Three-Phase Induction Motor	242
			6.6.1	Voltage Variations and Unbalance	243
			6.7	Three-Phase Induction Motor Model	244
			6.8	Assessment of Voltage Unbalance	245

Bibliography