



40TH ANNIVERSARY

ELECTRICITY

FOR REFRIGERATION, HEATING AND AIR CONDITIONING

9TH EDITION

RUSSELL E.
SMITH


40TH ANNIVERSARY

9TH EDITION

ELECTRICITY

FOR REFRIGERATION, HEATING, AND AIR CONDITIONING

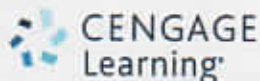RUSSELL E. SMITH
Athens Technical College



Australia • Brazil • Japan • Korea • Mexico • Singapore • Spain • United Kingdom • United States

CONTENTS

Preface	vii
1 Electrical Safety	1
Objectives 1 Key Terms 1 Introduction 2 1.1 Electrical Injuries 3 1.2 Dealing with Shock Victims 7 1.3 National Electrical Code® 8 1.4 Electrical Grounding 9 1.5 Circuit Protection 12 1.6 Circuit Lockout Procedures 15 1.7 Electrical Safety Guidelines 17 Summary 18 Review Questions 19	
2 Basic Electricity	21
Objectives 21 Key Terms 21 Introduction 22 2.1 Atomic Theory 22 2.2 Positive and Negative Charges 24 2.3 Flow Of Electrons 26 2.4 Conductors and Insulators 28 2.5 Electric Potential 29 2.6 Current Flow 31 2.7 Resistance 32 2.8 Electric Power and Energy 33 2.9 Ohm's Law 36 2.10 Calculating Electric Power 38 Summary 39 Review Questions 41	
3 Electric Circuits	43
Objectives 43 Key Terms 43 Introduction 44 3.1 Basic Concepts of Electric Circuits 44 3.2 Series Circuits 46 3.3 Parallel Circuits 50 3.4 Series-Parallel Circuits 54 Summary 57 Review Questions 58	
4 Electric Meters	60
Objectives 60 Key Terms 60 Introduction 61 4.1 Electric Meters 62 4.2 Ammeters 68 4.3 Voltmeters 72 4.4 Ohmmeters 75 Summary 79 Review Questions 80	
5 Components, Symbols, and Circuitry of Air-Conditioning Wiring Diagrams	82
Objectives 82 Key Terms 83 Introduction 83 5.1 Loads 84 5.2 Contactors and Relays 89 5.3 Magnetic Starters 91 5.4 Switches 92 5.5 Safety Devices 97 5.6 Transformers 99 5.7 Schematic Diagrams 100 5.8 Pictorial Diagrams 101 5.9 Installation Diagrams 102 Summary 105 Review Questions 106	
6 Reading Schematic Diagrams	109
Objectives 109 Key Terms 110 Introduction 110 6.1 Schematic Diagram Design 112 6.2 Reading Basic Schematic Diagrams 116 6.3 Reading Advanced Schematic Diagrams 137 Summary 161 Review Questions 162	

- 7 Alternating Current, Power Distribution, and Voltage Systems 165**
Objectives 165 Key Terms 165 Introduction 166 7.1 Basic Concepts of Alternating Current 166 7.2 Power Distribution 172 7.3 240-Volt-Single-Phase-60-Hertz Systems 173 7.4 Three-Phase Voltage Systems 175 7.5 240-Volt-Three-Phase-60-Hertz Delta System 176 7.6 208-Volt-Three-Phase-60-Hertz Wye System 178 7.7 Higher-Voltage Systems 179 Summary 182 Review Questions 183
- 8 Installation of Heating, Cooling, and Refrigeration Systems 185**
Objectives 185 Key Terms 185 Introduction 186 8.1 Sizing Wire 186 8.2 Disconnect Switches 194 8.3 Fusible Load Centers 199 8.4 Breaker Panels 200 8.5 Distribution Centers 203 8.6 Installing Electrical Circuits for Refrigeration, Heating, and Air-Conditioning Equipment 205 Summary 210 Review Questions 211
- 9 Basic Electric Motors 213**
Objectives 213 Key Terms 214 Introduction 214 9.1 Magnetism 214 9.2 Basic Electric Motors 218 9.3 Types of Electric Motors 220 9.4 Shaded-Pole Motors 223 9.5 Capacitors 227 9.6 Split-Phase Motors 232 9.7 Permanent Split-Capacitor Motors 238 9.8 Capacitor-Start-Capacitor-Run Motors 241 9.9 Three-Phase Motors 243 9.10 Electronically Commutated Motors 245 9.11 Hermetic Compressor Motors 251 9.12 Service Call Protocol 263 9.13 Service Calls 265 Summary 273 Review Questions 275 Practice Service Calls 279
- 10 Components for Electric Motors 282**
Objectives 282 Key Terms 282 Introduction 283 10.1 Starting Relays for Single-Phase Motors 283 10.2 Current or Amperage Relays 284 10.3 Potential Relays 286 10.4 Solid-State Starting Relays and Devices 292 10.5 Motor Bearings 298 10.6 Motor Drives 301 10.7 Service Calls 305 Summary 310 Review Questions 311 Practice Service Calls 314
- 11 Contactors, Relays, and Overloads 317**
Objectives 317 Key Terms 318 Introduction 318 11.1 Contactors 319 11.2 Relays 324 11.3 Overloads 330 11.4 Magnetic Starters 337 11.5 Push-Button Stations 341 11.6 Service Calls 342 Summary 347 Review Questions 349 Practice Service Calls 352
- 12 Thermostats, Pressure Switches, and Other Electric Control Devices 354**
Objectives 354 Key Terms 355 Introduction 355 12.1 Transformers 356 12.2 Thermostats 358 12.3 Staging Thermostats 378 12.4 Programmable Thermostats 382 12.5 Communicating Thermostats 385 12.6 Pressure Switches 388 12.7 Miscellaneous Electric Components 392 12.8 Service Calls 396 Summary 401 Review Questions 403 Practice Service Calls 406

- 13 Electronic Control Devices 409**
Objectives 409 Key Terms 409 Introduction 410 13.1 Electronic System Components 412 13.2 Basic Electronic Control Fundamentals 417 13.3 Simple Electronic Temperature Control 419 13.4 One-Function Electronic Controls 420 13.5 Electronic Timers 420 13.6 Electronic Devices for Electric Motors 423 13.7 Electronic Motor Protection Devices 423 13.8 Heat Pump Electronic Modules 425 13.9 Electronic Control Modules for Residential Gas Furnaces 429 13.10 Oil Furnace Electronic Controls 433 13.11 Troubleshooting Electronic Controls 433 Summary 435 Review Questions 436
- 14 Heating Control Devices 438**
Objectives 438 Key Terms 438 Introduction 439 14.1 Heating Fundamentals 440 14.2 Basic Heating Controls 443 14.3 Gas Heating Controls 450 14.4 Oil Heating Controls 465 14.5 Electric Heating Controls 471 14.6 Hydronic and Steam Controls 475 14.7 Service Calls 477 Summary 482 Review Questions 484 Practice Service Calls 487
- 15 Troubleshooting Electric Control Devices 489**
Objectives 489 Key Terms 489 Introduction 490 15.1 Electric Motors 490 15.2 Contactors and Relays 492 15.3 Overloads 494 15.4 Thermostats 500 15.5 Pressure Switches 503 15.6 Transformers 504 15.7 Electric Heating Controls 505 15.8 Gas Heating Controls 508 15.9 Oil Heating Controls 519 15.10 Service Calls 522 Summary 529 Review Questions 531 Practice Service Calls 534
- 16 Residential Air-Conditioning Control Systems 541**
Objectives 541 Key Terms 542 Introduction 542 16.1 Residential Air-Conditioning Equipment 544 16.2 Basic Residential Control Circuitry 549 16.3 Packaged Air-Conditioning Control Systems 561 16.4 Split-System Air-Conditioning Control Systems 570 16.5 Heat Pump Control Systems 576 16.6 Heat Pump Sequence of Operation 586 16.7 Advanced Residential Control Systems 591 16.8 Field Wiring 597 16.9 Check, Test, and Start Procedures 605 16.10 Customer Relations 608 Summary 610 Review Questions 612
- 17 Commercial and Industrial Air-Conditioning Control Systems 615**
Objectives 615 Key Terms 615 Introduction 616 17.1 Commercial and Industrial Heating and Air-Conditioning Equipment 617 17.2 Commercial and Industrial Control Circuitry 623 17.3 Commercial Condensing Unit 629 17.4 Commercial and Industrial Packaged Units 634 17.5 Air-Cooled Packaged Unit with Remote Condenser 636 17.6 Water-Cooled Packaged Units 640 17.7 Types of Total Commercial and Industrial Control Systems 641 17.8 Pneumatic Control Systems 644 17.9 Electronic Control Systems (Direct Digital Controls) 650 Summary 655 Review Questions 658

18	Troubleshooting Modern Refrigeration, Heating, and Air-Conditioning Control Circuitry and Systems	662
	Objectives 662 Key Terms 662 Introduction 663 18.1 Diagnosis of Electrical Components 664 18.2 Troubleshooting Tools 666 18.3 Troubleshooting with Electrical Meters 672 18.4 Using Troubleshooting Charts 682 18.5 Hopscotching: A Useful Tool for Troubleshooting 688 18.6 Troubleshooting Control Systems 697 18.7 Service Calls 701 Summary 708 Review Questions 709 Practice Service Calls 712	
	Appendix A	716
	Appendix B	717
	Glossary	718
	Index	728

INDEX

A

- Accuracy of meters, 67
- Adapters, grounding, 10
- Advanced control loops, 643
- Air-conditioners
 - circuit installation, 205-210
 - electrical connections, 209
 - heat pumps, 148-155
 - light commercial, 138-140
 - lockout relays, 141-144
 - packaged units, 132-137
 - SEER, 544
 - thermostats, 144-148
 - window units, 120-123
- Air-cooled packaged units, 546, 636-640
- Air supply sources, split-systems, 574-576
- Air-to-air heat pumps, 568, 580
- Alignment
 - contactors, 492-494
 - V-belts, 304
- Alternating current (AC), 21, 31
 - alternators, 169
 - basic concepts of, 166-172
 - cycles, 167-168
 - effective voltage, 168
 - electric motors, 220
 - inductance, 169-171
 - overview of, 166
 - phases, 169
 - power (wattage), 171-172
 - reactance, 169-171
 - single-phase, 173-175
 - three-phase, 175-176
 - voltage-current systems, 169
- Alternators, 165, 169
- Aluminum wire, 186
- American Wire Gauge, 185, 186
- Ammeters, 60, 61, 68-72
- Amperage
 - full-load amperage (FLA), 282, 284
 - locked rotor, 282, 284
 - relays, 284-286
- Amperes, 21, 30, 68-72
- Analog meters, 60, 64
- Anticipators, 355
 - cooling, 373-375

- heating, 371-373
 - thermostats, 370-375
- Anti-short-cycling timers, 409, 422, 615, 629
- Applications
 - contactors, 319-320
 - parallel circuits, 50-51
 - relays, 325-328
 - series circuits, 46-48
 - series-parallel circuits, 55-57
 - thermostats, 358-361, 382
- Armatures
 - contactors, 321
 - relays, 329
- Atomic energy, 172
- Atomic theory, 22-24
- Atoms, 21, 22

B

- Back electromotive force, 282
- Balance points, 110, 150
- Ball bearings, 282, 298-299
- Basic electricity
 - atomic theory, 22-24
 - conductors, 28-29
 - current flow, 31-32
 - electric potential, 29-31
 - electric power, 33-36, 38-39
 - energy, 33-36
 - flow of electrons, 26-28
 - insulators, 28-29
 - Ohm's law, 36-38
 - positive/negative, 24-25
 - resistance, 32-33
- Batteries, dry cell, 26
- Bearings, 282, 298-300
 - ball, 298-299
 - sleeve, 282, 299-300
- Bimetal
 - overloads, 333
 - thermostats, 363-365
- Blower motor circuits, 625-627
- Blower units, 619
- Boilers, hot water, 442, 619-620
- Breaker panels, 185, 200-203
- Breakers, 185, 199
- Break timers, 420-421

- Broken circuits, 44
- Burns, electrical, 6
- C**
- Cad cells, 438, 454, 466-469, 521-522, 559
- Calculating
 - electric power, 38-39, 40
 - output, 34
 - parallel circuits, 52-54
 - series circuits, 48-50
 - voltage drop, 192-194
- Capacitive reactance, 165, 171
- Capacitors, 214, 227-232
- Capacitor-start-capacitor-run motors, 214, 241-243
- Capacitor-start-induction-run motors, 236-237
- Capacitor-start motors, 214, 235
- Capacity control, 623
- Cardiopulmonary resuscitation (CPR), 1, 8
- Centrifugal switches, 236, 566
- Characteristics
 - of parallel circuits, 52-54
 - of series circuits, 48-50
- Charts
 - troubleshooting, 662, 668-672, 682-688
 - wire-sizing, 182
- Check, test, and start procedures, 542, 605
- Chemical means, 26-27
- Chillers, water, 621-623
- Circuit breakers, 1, 13, 495
- Circuit lockouts, 15-17
- Circuit protection, 12-15
- Circuits
 - anti-short-cycling timers, 629
 - blower motor, 625-627
 - commercial air-conditioning, 623-629
 - compressors, 550, 629-632
 - condenser fan motors, 551, 627, 632
 - fan switches, 447
 - ground fault circuit interrupter (GFCI), 11
 - hopscothching, 688-697
 - limit switches, 449, 450
 - live electrical, 1, 2
 - rectifiers, 415
 - residential air-conditioning, 549-560
 - safety controls, 554, 632-634
 - schematic diagram, 100, 113
 - short, 75
 - water chillers, 625
- Clamp-on ammeters, 60, 61, 69
- Closed circuits, 43, 44
- Closed electric motors, 222-223
- Coal, generating electricity, 172
- Code
 - circuit protection, 12-15
 - grounds, 9-12
 - National Electrical Code (NEC), 8
- Coils, 318
 - contactors, 321
 - solenoids, 87
 - troubleshooting, 322, 493
- Combustion chambers, 110, 130
- Commercial air-conditioning, 615, 616-617
 - air-cooled, 636-640
 - circuits, 623-629
 - condensing units, 629-634
 - electronic control systems, 650-655
 - equipment, 617-623
 - packaged, 634-635
 - pneumatic control systems, 644-650
 - types of, 641-644
 - water-cooled packaged units, 640-641
- Commercial condensing units, 618-619
- Commercial freezer schematic diagrams, 126-129
- Commercial heating equipment, 617-623
- Commercial refrigeration systems, 155-161
- Communicating thermostats, 355, 385-388
- Components for control systems, 318
 - contactors, 319-324
 - magnetic starters, 337-341
 - overloads, 330-337
 - push-button stations, 341-342
 - relays, 324-330
- Components for electric motors
 - amperage relays, 284-286
 - bearings, 298-300
 - current relays, 284-286
 - motor drives, 301-304
 - potential relays, 286-291
 - service calls, 305-310
 - solid-state relays, 292-298
 - starting relays, 283-284
- Compounds, 21, 23
- Compressors, 85
 - circuits, 629-632
 - control circuits, 550
 - hermetic, 214, 251-263
 - internal overload, 318
 - motor controls, 623-625
 - solid-state relays, 293
- Computer monitoring, 655
- Condenser fan motor circuits, 85, 551, 627, 632
- Condensing units, 542, 544, 570-574, 618-619
 - commercial air-conditioning, 629-634
 - power supply, 598
 - three-phase connections, 600
 - water-cooled, 615

- Conductors, 1, 5, 21–29, 216
 - Conduits, 205
 - Connections
 - condensing units, 600
 - diagrams, 110
 - Construction
 - ECMs, 248–249
 - relays, 328–329
 - Contactors, 83, 89–91, 104, 318, 319–324, 489, 550
 - applications, 319–320
 - coils, 321
 - contacts, 322
 - diagnostics, 665–666
 - electromagnets, 217
 - operations, 320–321
 - repairing, 323–324
 - symbols, 114
 - troubleshooting, 322–324, 492–494
 - Contacts, 90, 91, 318, 322
 - relays, 328
 - troubleshooting, 323, 492
 - Continuity, 60, 75, 79
 - Continuous ignition systems, 451
 - Control circuits, 43, 46, 47
 - Control devices (electric heat), 471–475, 505–508
 - Control devices (electronic), 409, 410–412
 - basic fundamentals, 417–419
 - for electric motors, 423
 - heat pumps, 425–428
 - oil furnaces, 433
 - one-function, 420
 - protection devices, 423–425
 - timers, 420–422
 - troubleshooting, 433–435
 - Control devices (gas heat), 508–518
 - Control devices (heating)
 - fundamentals, 440–443
 - gas controls, 450–465
 - oil heating, 465–471
 - Control devices (hydroponics and steam), 475–477
 - Control devices (oil heating), 519–522
 - Controlling elements, thermostats, 355, 361–370
 - Control loops, 615, 642, 643
 - Control relays, 110
 - Control systems (commercial air-conditioning), 615, 616–617
 - air-cooled with remote condensers, 636–640
 - circuits, 623–629
 - condensing units, 629–634
 - electronic control systems, 650–655
 - equipment, 617–623
 - packaged, 634–635
 - pneumatic control systems, 644–650
 - types of, 641–644
 - water-cooled packaged units, 640–641
 - Control systems (electric), 318
 - contactors, 319–324
 - magnetic starters, 337–341
 - overloads, 330–337
 - push-button stations, 341–342
 - relays, 324–330
 - service calls, 342–347
 - Control systems (residential air-conditioning), 541–544
 - advanced control systems, 591–597
 - check, test, and start procedures, 605–607
 - circuits, 549–560
 - customer relations, 608–610
 - equipment, 544–549
 - field wiring, 597–605
 - heat pumps, 576–590
 - packaged units, 561–570
 - split system, 570–576
 - Control systems, troubleshooting, 697–701
 - Control wiring, 542, 597, 601–605
 - Cooling. *See also* Air-conditioners
 - anticipators, 373–375
 - cycles (heat pumps), 586, 589
 - operations, multistage thermostats, 148
 - Copper wire, 186
 - Couplings, direct drives, 301–302
 - Current flow, 4, 31–32
 - circuits, 44. *See also* Electrical circuits
 - magnetic fields, 63
 - measurement of, 30, 68
 - parallel circuits, 52–54
 - series circuits, 48–50
 - Currents, 21, 31, 40
 - overload, 318, 335
 - relays, 282, 284–286
 - voltage-current systems, 169
 - Current-sensing lockout relays, 662
 - Customer relations, 542, 608–610
 - Customer service, 263–265
 - Cycles
 - alternating current (AC), 167–168
 - anti-short-cycling timers, 615
 - of basic electric motors, 219
 - defrost, 110, 125, 129, 150
 - of operations (heat pumps), 578
 - pump-down control systems, 155–161
 - short, 110, 141
- ## D
- Dampers, zones, 635
 - De-energized (relays), 83, 90
 - Defrost controls (heat pumps), 560, 581–584

- Defrost cycles, 110, 125, 129, 150, 568
 - Defrost modules, 409
 - Dehumidifiers, 110, 117-120
 - Delay-on-make timers, 420-421
 - Delays, time-delay control (TDC), 566
 - Delta systems, 165, 176-178
 - Delta windings, 214, 244
 - Design, schematic diagrams, 112-116
 - Devices, 84-89. See also Loads
 - Diagnostics. See Troubleshooting
 - contactors, 665-666
 - control systems, 697-701
 - electrical components, 664-666
 - motors, 664-665
 - relays, 665-666
 - switches, 665
 - Diagrams
 - connection, 110
 - electrical wiring, 667-668
 - factual, 101
 - fault isolation, 662, 684
 - installation, 83, 102-104, 110
 - ladder, 110
 - pictorial, 83, 101-102, 103
 - schematic. See Schematic diagrams
 - wiring. See Wiring
 - Differentials, 355, 391
 - Digital meters, 60, 64
 - Digital thermostats, 355, 366-367
 - Dimensions, electric motors, 223
 - Diodes, 414-415
 - Direct current (dc), 21, 31
 - overview of, 166
 - power distribution, 172-173
 - Direct digital control systems, 615, 650-655
 - Direct drives, 282, 301-302
 - Direct ignition burner control system, 459-462, 516-518
 - Discharge line thermostat (DLT), 633
 - Disconnect switches, 83, 94, 185, 194-198
 - fusible, 185
 - nonfusible, 185
 - Distribution centers, 185, 203-204, 211
 - Double insulated, 1, 11
 - Drives, motors, 301-304
 - Drop, voltage, 49, 187, 192-194
 - Dry cell batteries, 26
 - parallel circuits, 50-54
 - series circuits, 46-50
 - series-parallel circuits, 54-57
 - Electrical components (heat pumps), 579
 - Electrical components, diagnostics, 664-666
 - Electrical grounding, 9-12
 - Electrical meters, 666, 672-682
 - Electrical resistance heaters, 442, 585
 - Electrical safety. See Safety
 - Electrical shocks, 1, 3, 6, 7-8
 - Electrical wiring diagrams, 667-668
 - Electric energy, 21
 - Electric furnaces, 442, 542
 - Electric heat
 - control devices, 471-475
 - troubleshooting controls, 505-508
 - Electricity, 21, 25
 - static, 26
 - through chemical means, 26-27
 - through magnetism, 27-28
 - Electric meters
 - ammeters, 68-72
 - ohmmeters, 75-79
 - overview of, 61-67
 - voltmeters, 72-75
 - Electric motors, 213
 - basic, 218-220
 - capacitors, 227-232
 - capacitor-start-capacitor-run, 241-243
 - closed, 222-223
 - components for. See Components for electric motors
 - control devices for, 423
 - dimensions, 223
 - electronically commutated motors (ECMs), 245-251
 - hermetic compressors, 251-263
 - magnetism, 214-217
 - open, 222-223
 - permanent split-capacitor (PSC), 238-241
 - protection devices, 423-425
 - service calls, 263-272
 - shaded-pole motors, 223-227
 - speed, 221-222
 - split-phase, 232-238
 - strength, 221
 - three-phase, 243-245
 - troubleshooting, 490-492
 - types of, 220-223
 - Electric potential, 29-31
 - Electric power, 21, 33-36, 38-39, 40
 - Electric pressure, 21, 30
 - Electrodes, 21, 26
 - Electrolytes, 21, 26, 27
 - Electromagnets, 214, 216
- E**
- Effective voltage, 165, 168
 - Electrical circuits, 1, 43. See also Circuits
 - basic concepts of, 44-46
 - installation, 205-210
 - overview of, 44

- Electromotive force, 1, 3, 29, 40
- Electronically commutated motors (ECMs), 214, 245–251
- Electronic control devices, 409, 410–412
 - basic fundamentals, 417–419
 - electric heat, 471–475
 - for electric motors, 423
 - heat pump electronic modules, 425–428
 - hydroponics and steam, 475–477
 - oil furnaces, 433
 - one-function, 420
 - protection devices (electric motors), 423–425
 - residential gas furnaces, 429–432
 - service calls, 477–482
 - simple temperature control, 419
 - timers, 420–422
 - troubleshooting, 433–435
- Electronic control systems, 615, 650–655
- Electronic digital programmable thermostats, 385
- Electronic gas furnace control modules, 409
- Electronic motor overloads, 409
- Electronic resistance heaters, 438
- Electronic self-diagnostic features, 662, 672
- Electronic system components, 412–417
 - diodes, 414–415
 - light-emitting diodes (LEDs), 416–417
 - rectifiers, 414–415
 - semiconductors, 412–414
 - thermistors, 417
 - transistors, 415–416
 - triacs, 416
- Electronic timers, 409
- Electrons, 21
 - excess, 29, 30
 - flow, 26–28, 216
 - magnetism, 28
- Elements, 21, 22
- Emissions, 222
- Enclosed capacitor split-phase motors, 237–238
- Enclosures, 197
- Energized (relays), 83, 90
- Energy, 33–36
- Energy efficiency ratings, 544
- Energy-efficient electric motors, 222
- Energy Policy Act (1992), 222
- Equipment
 - air-conditioning (residential), 544–549
 - heating (commercial), 617–623
- Evaporators, 548, 551–553, 577
- Exterior overload, 254

- F**
- Factory-installed wiring, 542, 597
- Factual diagrams, 83, 101

- Failures. See Troubleshooting
- Fan-coil units, 542, 548–549
- Fan cycle control (FCC), 567
- Fan draft motor (FDM), 566
- Fan draft relay (FDR), 566
- Fan motors, evaporator control circuits, 551–553
- Fans
 - condenser, 85
 - controls, 443–447
 - switches, 438
- Fault isolation diagrams, 662, 684
- Field of force, 21, 29
- Field wiring, 542, 597–605
- Fire eye sensors, 454
- Flow
 - current, 4
 - electrons, 26–28, 216
 - reversals, 167
- Flux, 214, 215
- Force, field of, 29
- Formulas. See also Calculating
 - parallel circuits, 53–54
 - series circuits, 49–50
- Free electrons, 21, 25
- Frequency, 165, 167–168
- Full-load amperage (FLA), 282, 284
- Furnaces. See also Heating
 - control boards, 462–465
 - control systems, 549, 554–556
 - electric, 442
 - evaporators, 548
 - fossil fuel, 585
 - gas, 110, 129–132, 441
 - oil, 441, 558
 - power supply, 598
 - terminal boards, 603
- Fuses, 1, 13, 83, 97, 318
 - overloads, 330–331
 - sizes, 186
 - sizing, 600–601
 - troubleshooting, 495
- Fusible disconnect switches, 185, 197–198, 206
- Fusible load centers, 185, 199–200

- G**
- Gas
 - generating electricity, 172
 - valves, 438, 509–512
- Gas control devices (heating), 450–465, 508–518
- Gas furnaces, 110, 441, 542. See also Pilots
 - diagnostic codes, 678
 - electronic control modules, 409
 - ignition controls, 411

- pressure switches, 451
 - schematic diagrams, 129–132, 557
 - Gas heat electric packaged air-conditioning units, 564–568
 - Gas packs, 545
 - General Electric (GE) potential relay, 290
 - Green technology
 - electric motors, 222
 - electronically commutated motors (ECMs), 251
 - energy efficiency ratings, 544
 - hermetic compressors, 253
 - hybrid heat pump systems, 579
 - mercury disposal, 377
 - multistage equipment, 378
 - polychlorinated biphenyls (PCBs), 232
 - programmable thermostats, 385
 - zoned air-conditioning systems, 597
 - Ground fault circuit interrupters (GFCIs), 1, 11
 - Grounding adapters, 10
 - Grounds, 1, 9–12
 - Guidelines, safety, 17–18
- ## H
- Hard-start kits, 289
 - Heaters, 83, 88, 585
 - Heating
 - anticipators, 371–373
 - commercial equipment, 617–623
 - electrical circuit installation, 205–210
 - modes (heat pumps), 589
 - multistage thermostats, 144–148
 - Heating control devices, 438, 439–440
 - basic controls, 443–450
 - fundamentals, 440–443
 - gas controls, 450–465
 - oil heating, 465–471
 - Heat pumps, 110, 148–155, 542, 545
 - air-to-air, 568, 586
 - control modules, 409, 556–560
 - defrost controls, 411, 560, 581–584
 - electrical components, 579
 - electrical connections, 209
 - electronic modules, 425–428
 - HSPF (Heating Seasonal Performance Factor), 544
 - hybrid systems, 579
 - packaged air-conditioning units, 568–570
 - residential air-conditioning, 576–590
 - reversing valves, 579–581
 - sequence of operations, 586–590
 - staging thermostats, 381–382
 - supplementary heat, 585
 - water source, 568, 569, 570
 - water-to-air-heat pumps, 568
 - Hermetic compressors, 214, 251–263
 - Hertz (Hz), 168
 - Higher-voltage systems, 179–182, 183
 - High-pressure switches, 125, 355, 390, 633
 - Hopscotching, 662, 688–697
 - Hot surface ignition, 438, 459, 557
 - Hot water boilers, 442, 615, 619–620
 - HSPF (Heating Seasonal Performance Factor), 544
 - Humidistats, 355, 392
 - Hybrid heat pump systems, 579
 - Hydrogen atoms, 23
 - Hydroponics control devices, 475–477
 - Hydropower, generating electricity, 172
- ## I
- Ignition controls (gas furnaces), 411
 - Ignition modules, 409, 438, 455, 489, 516
 - Impedance, 165, 171, 182
 - Induced magnetism, 214, 216–217
 - Inductance, 165, 169–171
 - Inductive loads, 318, 322, 330
 - Inductive reactance, 165, 171
 - Industrial air-conditioning/heating, 617. *See also*
 - Commercial air-conditioning/heating
 - Industrial condensing units, 618–619
 - Injuries, 3–8
 - Installation
 - breaker panels, 200–203
 - diagrams, 83, 102–104, 110
 - disconnect switches, 194–198
 - distribution centers, 203–204
 - electrical circuits, 205–210
 - fusible load centers, 199–200
 - instructions, 662, 668
 - overview of, 186
 - packaged air-conditioning units, 547
 - programmable thermostats, 384–385
 - thermostats, 375–376
 - wire size, 186–194
 - Insulators, 21, 28–29
 - Interlocks, 615, 625, 627–628
 - Intermittent pilot burner control system, 453–458, 513–515
 - Internal compressor overload, 318, 333
 - Internal overload, 255, 498–499
- ## K
- Kilowatthours (kWh), 21, 34, 40
- ## L
- Ladder diagrams, 110
 - Law of electric charges, 21, 25
 - Light commercial air-conditioning systems, 110, 138–140
 - Light-emitting diodes (LEDs), 409, 416–417

- Lights, signal, 83, 88
 - Limit switches, 110, 130, 447-448
 - Line break overload, 318, 332
 - Line-voltage
 - control systems, 110, 117
 - overloads, 496
 - thermostats, 355, 367-368, 500-501
 - Live electrical circuits, 1, 2
 - Loads, 83, 84-89
 - circuits, 44
 - fusible load centers, 185, 199-200
 - heaters, 88
 - inductive, 318, 322, 330
 - motors, 85-87. *See also* Motors
 - parallel circuits, 50
 - resistive (noninductive), 318, 322, 330
 - signal lights, 88
 - solenoids, 87
 - symbols, 104, 114
 - Locked rotor amperage, 282, 284
 - Lockout relays, 110, 141-144
 - Lockouts, circuit, 15-17
 - Low-pressure boilers, 442
 - Low-pressure switches, 125, 355, 390-391, 633
 - Low-voltage control systems, 110, 113, 129
 - Low-voltage thermostats, 355, 362, 368-370, 501-502
 - Lubrication, sleeve bearings, 299-300
- M**
- Made circuits, 44
 - Magnetic fields, 60, 62, 63, 214, 215
 - alternating circuit (AC), 169
 - ammeters, 69
 - voltmeters, 73
 - Magnetic overload, 83, 97, 318, 335
 - Magnetic relays, 282, 284
 - Magnetic starters, 83, 91-92, 318, 337-341
 - operations, 339-340
 - troubleshooting, 340-341
 - types of, 339-340
 - Magnetism, 27-28, 214-217
 - Main valve (MV), 567
 - Manual switches, 94
 - Matter, 21, 22
 - Measurable resistance, 60, 75
 - Measurement
 - current flows, 30, 68
 - microfarads, 227
 - resistance, 75
 - Mechanical linkage, 318
 - contactors, 322, 323
 - relays, 329
 - troubleshooting, 494
 - Medical assistance, shock victims, 7-8
 - Mercury bulb thermostats, 365
 - Mercury disposal, 377
 - Meters. *See also* Electric meters
 - accuracy of, 67
 - analog, 64
 - differences among, 64-67
 - digital, 64
 - electrical, 672-682
 - volt-ohm, 72, 76
 - Microfarads, 214, 227, 230
 - Modules, defrost, 409
 - Molecules, 21, 22
 - Monitoring buildings/computers, 655
 - Motors, 83, 85-87, 489. *See also* Electric motors
 - blower motor circuits, 625-627
 - compressor controls, 623-625
 - condenser fan motor circuits, 627, 632
 - diagnostics, 664-665
 - drives, 301-304
 - electronic motor overloads, 409
 - evaporator control circuits, 551-553
 - fan draft motor (FDM), 566
 - troubleshooting, 490-492
 - Multifunction electronic motor protectors, 425
 - Multistage thermostats, 110, 144-148
- N**
- National Electrical Code (NEC), 1, 8, 185, 186, 187
 - circuit protection, 12-15
 - grounds, 9-12
 - wire-sizing charts, 182
 - National Electrical Manufacturers' Association (NEMA), 222
 - Negative charges, 24-25
 - Neutrons, 21, 23
 - Nonfusible disconnect switches, 185, 197-198
 - Noninductive loads, 330
 - Normally (contacts), 83, 90
 - Normally closed (contacts), 83, 90, 91
 - Normally open (contacts), 83, 90, 91
 - Notation, pressure switches, 391-392
 - Nucleus, 21, 23, 39
- O**
- Ohmmeters, 60, 64, 75-79
 - Ohms, 21, 30
 - Ohm's law, 21, 36-38
 - parallel circuits, 53
 - voltage drop calculations, 50
 - Oil
 - generating electricity, 172
 - sleeve bearings, 299-300
 - Oil furnaces, 433, 441, 542, 558
 - Oil heating controls, 465-471, 519-522
 - Oil safety switches, 355, 392-394

- One-function control devices, 420
- Open circuits, 43, 44, 60, 75
- Open electric motors, 222–223
- Open-type electric motors, troubleshooting, 491
- Operations
 - capacitor-start-capacitor-run motors, 241–242
 - contactors, 320–321
 - current relays, 284–286
 - electronically commutated motors (ECMs), 249–250
 - heat pumps, 578, 586–590
 - hermetic compressors, 252–253
 - magnetic starters, 339–340
 - permanent split-capacitor (PSC) motors, 239–240
 - potential relays, 286–288
 - shaded-pole motors, 224–225
 - solid-state starting relays, 296–298
 - split-phase motors, 234–235
 - staging thermostats, 379–380
 - three-phase motors, 244
 - transformers, 356–357
- Output, calculating, 34
- Overloads, 97, 318, 330–337
 - bimetal, 333
 - currents, 318, 335
 - electronic motor, 409
 - exterior, 254
 - fuses, 330–331
 - internal, 255, 498–499
 - internal compressor, 318, 333
 - line break, 318, 332
 - line voltage, 496
 - magnetic, 318, 335
 - pilot duty, 318, 332, 335, 496–498
 - protection, 423–424
 - thermal, 83
 - troubleshooting, 337, 494–499
- Oxygen atoms, 23
- P**
- Packaged air-conditioning units, 544, 545–547, 561–570
 - commercial, 634–635
 - gas heat electric, 564–568
 - heat pumps, 568–570
 - power supply, 599
 - schematic diagrams, 132–137
- Package units, 542
- Panels
 - breaker, 200–203
 - breakers, 199
- Parallel circuits, 43, 44, 50–54
 - applications, 50–51
 - characteristics of, 52–54
 - schematic diagrams, 115
- Peak voltage, 165, 168
- Permanent magnets, 214, 216
- Permanent split-capacitor (PSC) motors, 214, 238–241, 293, 294
- Phase reversal protector, 425
- Phases, 165, 169
- Pictorial diagrams, 83, 101–102, 103
- Pilot relight control (PRC), 566, 567
- Pilots, 438, 439
 - adjusting flames, 509
 - assemblies, 438, 455
 - direct ignition burner control system, 516–518
 - duty devices, 83, 97
 - duty overload, 318, 332, 335, 496–498
 - intermittent pilot burner control system, 513–515
- Pilot valve (PV), 567
- Pneumatic control systems, 615, 644–650
- Poles, 90
 - magnetism, 215
 - shaded-pole motors, 223–227
 - of stators, 220
- Polychlorinated biphenyls (PCBs), 232
- Positive charges, 24–25
- Positive temperature coefficient (PTC), 284
- Potential difference, 29
- Potential relays, 282, 286–291
- Power
 - circuits, 43, 50
 - distribution, 172–173
 - factor, 22, 33, 40, 165
 - wattage, 171–172
- Power supply
 - condensing units, 598
 - to furnaces, 598
 - packaged air-conditioning units, 599
 - schematic diagrams, 100, 113
 - series circuits, 47
- Power wiring, 542, 597–600
- Pressure, electric, 30
- Pressure switches, 83, 96, 355, 388–392, 448–450, 489
 - gas furnaces, 451
 - troubleshooting, 392, 503–504
- Primary controls, 438, 465
 - cad cell troubleshooting, 521–522
 - stack switch troubleshooting, 519–521
- Programmable thermostats, 355, 382–385
 - applications, 382–384
 - electronic digital, 385
 - installation, 384–385
- Protection devices for electric motors, 423–425
- Protons, 22, 23
- Pump-down control systems, 110, 155–161
- Push-button stations, 318, 341–342
- Push-button switches, 83, 94, 95

R

- Range, 355, 391
- RBM potential relays, 291
- Reactance, 165
- Reading
 - advanced schematic diagrams, 137-161
 - basic schematic diagrams, 116-137
- Rectifiers, 409, 414-415
- Redundant-type gas valves, 511
- Refrigerant 22 (R-22), 23
- Refrigeration, electrical circuit installation, 205-210
- Relays, 83, 89-91, 104, 318, 324-330, 489
 - amperage, 284-286
 - applications, 325-328
 - construction, 328-329
 - control, 110
 - currents, 282, 284-286
 - current-sensing lockout, 662
 - diagnostics, 665-666
 - fan draft relay (FDR), 566
 - lockout, 110, 141-144
 - magnetic, 284
 - potential, 282, 286-291
 - for single-phase motors, 283-284
 - solid-state, 282, 292-298
 - symbols, 114
 - time-delay, 355, 394, 446
 - troubleshooting, 330, 492-494
- Remote bulb thermostats, 362-363
- Remote condensers, 636-640
- Repairing contactors, 323-324
- Replacing capacitors, 229
- Residential air-conditioning, 541-544
 - advanced control systems, 591-597
 - check, test, and start procedures, 605-607
 - circuits, 549-560
 - customer relations, 608-610
 - equipment, 544-549
 - field wiring, 597-605
 - heat pumps, 576-590
 - packaged air-conditioning units, 561-570
 - split system, 570-576
- Residential gas furnace control devices, 429-432
- Resistance, 22, 32-33, 40
 - measurement, 75
 - parallel circuits, 52-54
 - series circuits, 48-50
- Resistance-start-induction-run motors, 232-234
- Resistive (noninductive) load, 318, 322, 330
- Reversing
 - flow, 167
 - shaded-pole motors, 226
 - valves, 110, 148, 542, 577, 579-581, 582

- Rotating turbines, 172
- Rotors, 214, 218
 - locked amperage, 284
 - squirrel cage, 214, 220
- Running capacitors, 214, 228

S

- Safety, 2-3
 - devices, 97-99
 - guidelines, 17-18
 - shutoffs, 512
- Safety controls
 - circuits, 554, 632-634
 - symbols, 114
- Schematic diagrams, 83, 100-101
 - 208-volt-three-phase-60-Hz wye systems, 179
 - 240-volt-single-phase-60-Hz systems, 174
 - 240-volt-three-phase-60-Hz delta systems, 176-178
 - 277/480-volt systems, 181
 - advanced, 137-161
 - air-conditioning systems controlled by multistage thermostats, 144-148
 - air-conditioning systems with lockout relays, 141-144
 - air-cooled packaged units with remote condensers, 638, 639
 - air-to-air heat pumps, 580
 - anti-short-cycling timers, 422
 - basic, 116-137
 - capacitors, 230
 - capacitor-start-capacitor-run motors, 242
 - commercial condensing units, 630
 - commercial freezers, 126-129
 - condensing units, 575
 - contactors, 320, 550
 - current relays, 285, 286
 - defrost circuits (heat pumps), 584
 - dehumidifiers, 117-120
 - delay-on-make timers, 421
 - design, 112-116
 - digital thermostats, 367
 - distribution centers, 204
 - electronic control modules (heat pumps), 427
 - evaporator fan motors, 553
 - fan motors, 552
 - fusible disconnect switches, 196
 - gas furnaces, 129-132, 557
 - gas heat electric packaged air-conditioning units, 567, 568
 - hard-start kits, 289
 - heat pumps, 148-155, 587, 588, 590, 691
 - ignition modules (gas furnaces), 430
 - light commercial air-conditioning systems, 138-140

- line break overloads, 332
- magnetic overloads, 336
- magnetic starters, 339
- mechanical electrical control systems, 644
- oil furnaces, 558
- overloads, 331
- overview of, 110–112
- packaged air-conditioning units, 132–137, 562, 563
- potential relays, 288
- pump-down control systems, 155–161
- relays, 325, 326, 327
- shaded-pole motors, 225
- simple window air conditioners, 120–123
- single-phase compressors, 253
- solid-state starting relays, 297
- split-phase motors, 237
- staging thermostats, 380
- thermostats, 360, 361
- three-phase motors, 244
- walk-in coolers, 123–126
- water-cooled condensing units, 628
- water-cooled packaged units, 641
- water source heat pumps, 570
- zone control systems, 596
- Sealed motors, troubleshooting, 491
- Seasonal energy efficiency ratio (SEER), 22, 36
- SEER (Seasonal Energy Efficiency Ratio), 544
- Semiconductors, 409, 412–414
- Sequence of operations (heat pumps), 586–590
- Sequencers, 438, 472, 473, 506
- Series circuits, 43, 44, 46–50
 - applications, 46–48
 - characteristics of, 48–50
- Series-parallel circuits, 43, 44, 54–57, 55–57
- Service calls
 - commercial refrigeration, 399–400
 - components for electric motors, 305–310
 - control systems, 342–347
 - electric motors, 263–272
 - electronic control devices, 477–482
 - industrial conditioned air system, 400–401
 - refrigerators, 397–398
 - residential conditioned air system, 396–397, 398–399
 - troubleshooting, 522–529, 701–707
- Service instructions, 662, 668
- Set points, 110, 120
- Shaded-pole motors, 214, 223–227
- Shocks, 1, 3, 6
- Shock victims, medical assistance for, 7–8
- Short circuits, 60, 75
- Short cycles, 110, 141
- Shutoffs, safety, 512
- Signal lights, 83, 88
- Simple temperature control, 419
- Simple window air conditioners, 120–123
- Sine waves, 165, 166, 167
- Single-phase, 165, 169, 424
- Single-phase alternating current (AC), 173–175
- Single-phase motors, starting relays for, 283–284
- Sizing
 - fuses, 600–601
 - transformers, 357–358
 - wire, 186–194, 600–601
- Sleeve bearings, 282, 299–300
- Snap action, 355, 364
- Solenoids, 83, 87, 155
 - reversing valves, 581
 - valves, 355, 395–396
- Solid state, 409, 412
- Solid-state relays, 282, 292–298
- Spark ignition, 438, 459
- Speed of electric motors, 221–222
- Spikes, voltage, 409, 418
- Split-phase motors, 214, 232–238
- Split system, 570–576
- Split systems, 542, 544, 547–549
- Squirrel cage rotors, 214, 220
- Stack switches, 438, 466, 467, 469–471, 519–521
- Staged systems, 378
- Staging thermostats, 355, 378–381
 - heat pumps, 381–382
 - operations, 379–380
- Standing pilot burner control systems, 451–453
- Starters
 - hard-start kits, 289
 - magnetic, 91–92, 318, 337–341
- Starting
 - capacitors, 214, 227
 - check, test, and start procedures, 605–607
 - relays, 282
 - single-phase motor relays, 283–284
- Star winding, 214, 244
- Static electricity, 22, 26
- Stators, 214, 218
- Steam boilers, 442
- Steam control devices, 475–477
- Stop-start push-button stations, 341
- Strength of electric motors, 221
- Supplementary heat (heat pumps), 585
- Switches, 83, 92–96
 - centrifugal, 236, 566
 - diagnostics, 665
 - disconnect, 83, 94, 185, 194–198
 - fans, 438, 443–447
 - fusible disconnect, 185, 197–198, 206

Switches (Continued)

- high-pressure, 125, 355, 390, 633
- limit, 110, 130, 447-448
- low-pressure, 125, 355, 390-391, 633
- nonfusible disconnect, 185, 197-198
- oil safety, 355, 392-394
- pressure, 83, 96, 355, 388-392, 448-450, 489, 503-504
- push-button, 83, 94, 95
- stack, 438, 466, 467, 519-521
- symbols, 114

Symbols, 83

- capacitors, 227
- contactors, 90, 104
- diodes, 414
- fuses, 97
- heaters, 88
- light-emitting diodes (LEDs), 416
- loads, 104
- magnetic starters, 92
- manual switches, 94
- motors, 86
- overload, 98, 99
- pressure switches, 96
- push-button switches, 95
- rectifiers, 414
- relays, 90, 104
- schematic diagrams, 114
- signal lights, 88
- switches, 93
- thermostats, 95
- transformers, 99
- triacs, 416

Systems

- 208-volt-three-phase-60-Hz wye systems, 178-179
- 240-volt-single-phase-60-Hz systems, 173-175
- 240-volt-three-phase-60-Hz delta systems, 176-178
- 277/480-volt systems, 180-182

T

- Temperature control, 419
- Terminal boards, furnaces, 603
- Terminal identification, 253-254
- Terms, pressure switches, 391-392

Testing

- capacitors, 231
- check, test, and start procedures, 605-607
- Thermal overload, 83, 97
- Thermistors, 409, 413, 417
- Thermocouples, 438, 452, 511
- Thermostats, 83, 94, 95, 358-377, 489
 - anticipators, 370-375
 - applications, 358-361

- bimetal, 363-365
- communicating, 355, 385-388
- controlling elements, 355, 361-370
- digital, 355, 366-367
- discharge line thermostat (DLT), 633
- electronic programmable, 410
- installation, 375-376
- line-voltage, 355, 367-368, 500-501
- low-voltage, 355, 362, 368-370, 501-502
- mercury bulb, 365
- multistage, 110, 144-148
- overview of, 355-356
- programmable, 355, 382-385
- remote bulb, 362-363
- staging, 355, 378-381
- troubleshooting, 376-377, 500-502
- wiring, 605

Three-phase, 165, 169

- alternating current (AC), 175-176
- connections (condensing units), 600
- motors, 214, 243-245

Three-prong plugs, 1, 10

Throw (switches), 83, 92

Time clocks, 355, 394-395

Time-delay control (TDC), 566

Time-delay relays, 355, 394, 446

Timers, 420-422

- anti-short-cycling, 409, 422, 615, 629
- break, 420-421
- delay-on-make, 420-421
- electronic, 409
- solid-state, 410

Tools

- charts, 668-672
- electrical meters, 666
- electrical wiring diagrams, 667-668
- electronic self-diagnostic features, 672
- hopscotching, 688-697
- installation instructions, 668
- service instructions, 668
- troubleshooting, 666-672

Torque, 214, 223

Transformers, 83, 99-100, 355, 356-358, 489

- operations, 356-357
- sizing, 357-358
- symbols, 114
- troubleshooting, 358, 504-505

Transistors, 409, 415-416

Trees, troubleshooting, 662, 684

Triacs, 409, 416

- Troubleshooting, 489
 - cad cells, 521-522
 - capacitors, 228-232

- capacitor-start-capacitor-run motors, 242–243
 - charts, 662, 668–672, 682–688
 - circuit breakers, 495
 - coils, 493–494
 - contactors, 322–324, 492–494
 - control systems, 697–701
 - current relays, 286
 - direct ignition burner control system, 516–518
 - with electrical meters, 672–682
 - electric heat controls, 505–508
 - electric motors, 490–492
 - electronically commutated motors (ECMs), 250–251
 - electronic control devices, 433–435
 - fuses, 495
 - gas control devices (heating), 508–518
 - hermetic compressors, 254–263
 - hopscotching, 688–697
 - intermittent pilot burner control systems, 513–515
 - internal overloads, 498–499
 - line voltage overloads, 496
 - line-voltage thermostats, 500–501
 - low-voltage thermostats, 501–502
 - magnetic starters, 340–341
 - mechanical linkage, 494
 - oil heating controls, 519–522
 - overloads, 337, 494–499
 - permanent split-capacitor (PSC) motors, 240–241
 - pilot duty overloads, 496–498
 - potential relays, 288–291
 - pressure switches, 392, 503–504
 - relays, 330, 492–494
 - schematic diagrams, 110
 - service calls, 522–529, 701–707
 - shaded-pole motors, 227
 - solid-state starting relays, 298
 - split-phase motors, 235–236
 - stack switches, 519–521
 - thermostats, 376–377, 500–502
 - three-phase motors, 245
 - tools, 666–672
 - transformers, 358, 504–505
 - trees, 662, 684
- Turbines, 172
- Two-stage heating, 586
- Types
- of circuits, 44
 - of commercial air-conditioning, 641–644
 - of disconnect switches, 206
 - of electric motors, 220–223
 - of fuses, 13, 97
 - of magnetic starters, 339–340
 - of meters, 64–67
 - of motors, 85
 - of pressure switches, 388
 - of solenoids, 87
 - of staging thermostats, 379–380
 - of starting relays, 283
 - of switches, 93
- U**
- Universal motor starting relays, 296
- V**
- Values, electrical shocks, 6
- Valves
- gas, 438, 509–512
 - main valve (MV), 567
 - pilot valve (PV), 567
 - reversing, 110, 148, 542, 577, 579–581, 582
 - solenoids, 355, 395–396
- Variable frequency drives (VFDs), 246
- Varistors, 409, 413
- V-belts, 282, 302–303
- Voltage, 29
- drops, 43, 49, 187, 192–194
 - effective, 165, 168
 - electrical meters, 679
 - higher-voltage systems, 179–182, 183
 - line-voltage control systems, 110
 - low-voltage control systems, 110
 - parallel circuits, 52–54
 - peak, 165, 168
 - series circuits, 47, 48–50
 - spikes, 409, 418
- Voltage-current systems, 169
- Voltage/Potential Difference/Electromotive Force, 22
- Voltmeters, 60, 64, 72–75
- Volt-ohm meters, 72, 76
- Volt-ohm-millimeters, 60, 61
- Volts, 22, 30
- W**
- Walk-in coolers, 123–126
- Water, atomic structure of, 23
- Water chillers, 615, 621–623, 625
- Water-cooled condensing units, 615, 627–628
- Water-cooled packaged units, 546, 640–641
- Water source heat pumps, 568, 569, 569, 570, 570
- Water-to-air heat pumps, 568
- Watts (W), 22, 33
- Windings
- electric motors, 219
 - shaded-pole motors, 224
 - split-phase motors, 235
- Window air conditioners, 120–123

Wiring

- control, 542, 597, 601-605
- electrical diagrams, 667-668
- factory-installed, 542, 597
- fan switches, 444
- field, 542, 597-605
- line-voltage thermostats, 368
- low-voltage thermostats, 369
- power, 542, 597-600

- programmable thermostats, 384
 - push-button stations, 341
 - wire size, 186-194, 600-601
- Wye systems, 165, 178-179, 244

Z

- Zones
- control systems, 592-597
 - dampers, 635